

上海交通大学试卷 (A 卷)

(2020 至 2021 学年 第 1 学期)


班级号 _____ 学号 _____ 姓名 _____

课程名称 EI243 数字电子技术 成绩 _____

PART I Multiple Choice (单选题, 40%)


1. The pulse width of the nonideal pulse in Figure 1 is defined by ().

(A) a (B) b (C) c (D) d

 

2. Figure 2 is an example of a () diagram.

 (A) circuit (B) logic (C) state (D) timing



3. In BCD addition, if a 4-bit sum is greater than 9, or if a carry out of the 4-bit group is generated, add () to the 4-bit sum.

(A) 2 (0010) (B) 4 (0100) (C) 6 (0110) (D) 8 (1000)

4. The OR operation is equivalent to ().

(A) Boolean addition (B) Boolean multiplication (C) Boolean negation (D) mod-2 addition

5. The data selection function is performed by a logic circuit called a/an ().

(A) decoder (B) demultiplexer (C) encoder (D) multiplexer

6. The logic expression $\overline{A}\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D$ is equivalent to ().

我承诺，我将严格遵守考试纪律。

承诺人：_____.

题号	I	II	III			
	1-20	21-32	33	34	/	/
得分					/	/
批阅人(流水阅卷教师签名处)					/	/

(A) $\overline{AC}(\overline{BD} + BD)$ (B) $\overline{AC} \overline{B} \oplus \overline{D}$ (C) $\overline{AC} \overline{\overline{BD} + \overline{BD}}$ (D) all of the above

7. () is a POS expression.

(A) $AB + CD$ (B) $\overline{\overline{A} + \overline{B} + \overline{C} + \overline{D}}$ (C) $(A + B)(C + D)$ (D) $\overline{\overline{A} \overline{B} \overline{C} \overline{D}}$

8. The AND operation is the dual of the () operation.

(A) NAND (B) negative OR (C) OR (D) none of the above

9. The logic expressions for the circuit in Figure 3 are (), and $Z = \overline{X + Y}$.

- (A) $X = \overline{A_1}B_1 + \overline{A_1} \oplus \overline{B_1} \overline{A_0}B_0, Y = \overline{A_1} \oplus \overline{B_1} \overline{A_0} \oplus \overline{B_0}$
- (B) $X = A_1\overline{B_1} + \overline{A_1} \oplus \overline{B_1} \overline{A_0}B_0, Y = \overline{A_1} \oplus \overline{B_1} \overline{A_0} \oplus \overline{B_0}$
- (C) $X = \overline{A_1}B_1 + (A_1 \oplus B_1) \overline{A_0}B_0, Y = (A_1 \oplus B_1)(A_0 \oplus B_0)$
- (D) $X = A_1\overline{B_1} + (A_1 \oplus B_1) \overline{A_0}B_0, Y = (A_1 \oplus B_1)(A_0 \oplus B_0)$

 


Figure 3

10. The logic expression for the circuit in Figure 4 is ().

- (A) $\overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}C + ABC$
- (B) $\overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}C + ABC$

(C) $\overline{A}\overline{B}\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + A\overline{B}C$

(D) none of the above

 


Figure 4

 


Figure 5

11. The expression for the circuit in Figure 5 is ().

(A) $\overline{A}\overline{B}\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + A\overline{B}C$

(B) $\overline{A}\overline{B}C + \overline{A}BC + A\overline{B}\overline{C} + ABC$

(C) $\overline{A}\overline{B}C + \overline{A}BC + A\overline{B}\overline{C} + ABC$

(D) none of the above

12. Consider the circuit in Figure 6. If $D = (D_2D_1D_0)_2$, $Y = (Y_4Y_3Y_2Y_1Y_0)_2$, then ().

(A) $Y = D$ (B) $Y = 2D$ (C) $Y = 3D$ (D) none of the above

 


Figure 6

13. A combinational circuit accepts a 2-bit number $A = (A_1A_0)_2$ and produces a 5-bit binary number

$X = (X_4X_3X_2X_1X_0)_2$. If $X = A^3$, then $X_4 = ()$.

(A) 0 (B) A_0 (C) A_1 (D) A_1A_0

14. Draw the Q output relative to the clock with the input as shown in Figure 7. Assume that Q is initially LOW. ()

- (A) a (B) b (C) c (D) none of the above

 


Figure 7

15. Draw the Q output relative to the clock with the inputs as shown in Figure 8. Assume that Q is initially LOW.

- (A) a (B) b (C) c (D) none of the above

 


Figure 8

16. Figure 9 shows the logic symbol for a () one-shot.

- (A) negative-edge triggered nonretriggerable
(B) negative-edge triggered retriggerable
(C) positive-edge triggered nonretriggerable
(D) positive-edge triggered retriggerable

 


Figure 9

 


Figure 10

17. Figure 10 shows a ().

- (A) D flip-flop (B) D latch (C) J-K latch (D) J-K flip-flop

18. In the general sequential logic model in Figure 11, the outputs of the memory are called the () variables of the sequential logic.

- (A) excitation (B) input (C) output (D) state

 


Figure 11

19. We need at least () flip-flops to design a counter to produce the following binary sequence: 0, 9, 1, 8, 2, 7, 3, 6, 0, ...

- (A) 4 (B) 3 (C) 2 (D) 1

20. For the cascaded counter configuration in Figure 12, the waveform at point () has a frequency of 1 kHz.

- (A) ① (B) ② (C) ③ (D) ④

 


Figure 12

PART II Filling Blanks (填空题, 36%)

21. Figure 13 shows the operation of a two-input () gate.

 


Figure 13

22. Convert the unsigned binary number 101 0110 to decimal. ()

23. Convert the decimal number 177.8125 to binary. ()

24. Determine the decimal value of the signed binary number in the 2's complement form:

1011 0001. ()

25. Add the two hexadecimal numbers: $1A58_{16}$ and $81D0_{16}$. ()

26. Determine the minimum expression for the circuit in Figure 14 .

()

 


Figure 14

27. Write the NOR-NOR expression for the truth in Figure 15. Minimization is not required.

()

28. Minimize the expression: $X = \overline{A}BD + \overline{A}\overline{B}CD + \overline{B}CD + \overline{A}\overline{B} + C(B + D)$.

()

29. Determine the even parity bit for the 7-bit group: 101 0111. ()

30. Determine the modulus of the cascaded counter in Figure 16. ()

A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Figure 15

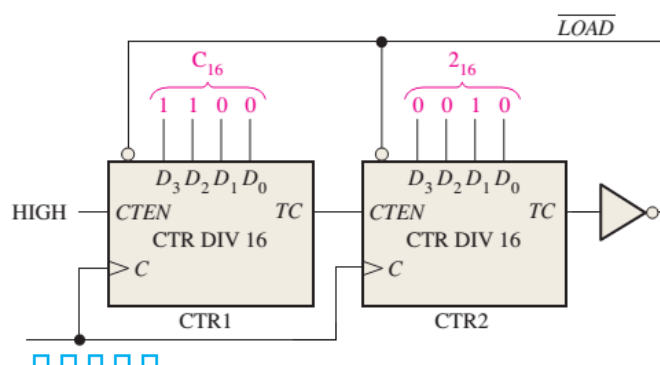


Figure 16

31. Determine the modulus of the counter in Figure 17. ()

 


Figure 17

 


Figure 18

32. Figure 18 shows a 2-bit asynchronous counter connected to a decoder (the AND gate). Decoding glitch can be seen when the counter state Q_1Q_0 changes from () to ().

PART III Design (设计题, 24%)

- 33.** Design a circuit with three input variables that will only produce a 1 output when two or three input variables are 1s. (9%)

 


Figure 19

- 34.** Design a synchronous counter with the binary count sequence 000, 001, 010, 011, 100, 000,
Use D flip-flops. (15%)