

2011-2012 Answer

1. (10%) Find the minimum POS form for the following expression

$$Y = \overline{(A \oplus B) \overline{B} (\overline{A} B C D + \overline{A} C D)}$$

Solution.

$$\begin{aligned} Y &= \overline{(A \oplus B) (B + (\overline{A} B C D + \overline{A} C D))} = \overline{(A \oplus B) (B + (\overline{A} + \overline{B} + C + D)(\overline{A} + \overline{C} + D))} \\ &= \overline{(A \oplus B) (B + A + D + (\overline{B} + C) \overline{C})} = \overline{(A \oplus B) (B + A + D + \overline{B} \overline{C})} \\ &= \overline{(A \oplus B) (A + B + \overline{C} + D)} = \overline{A \oplus B} + \overline{A + B + \overline{C} + D} \\ &= (\overline{A} \overline{B} + A B) + \overline{A} \overline{B} C \overline{D} = \overline{A} \overline{B} + A B = (A + \overline{B})(\overline{A} + B) \end{aligned}$$

2. (10%) Use the minimum number of gates to implement a circuit that detects if a 4-bit binary number $A_3 A_2 A_1 A_0$ is greater than 9. When the number is greater than 9, the output $Y = 1$; otherwise $Y = 0$.

Solution.


The Truth Table

Dec	A_3	A_2	A_1	A_0	Y
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	1
11	1	0	1	1	1
12	1	1	0	0	1
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1


The Karnaugh Map.

$A_3 A_2$	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	0	0	1	1
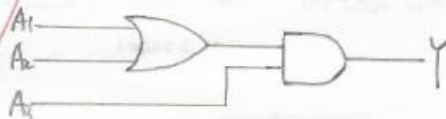
$$\begin{aligned} Y &= A_3 A_2 + A_3 A_1 \\ &= A_3 (A_1 + A_2) \end{aligned}$$



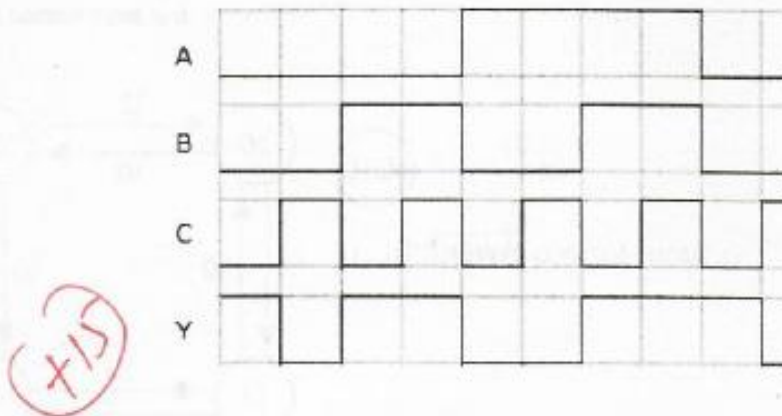
3. (15%) Use one 3-line-to-8-line decoder 74LS138 and one NAND gate to implement a circuit whose output Y and inputs A, B, and C are related as shown in Figure 1.



(a) Waveforms for the desired circuit

INPUTS					OUTPUTS							
S ₁	$\overline{S_2 + S_3}$	A ₂	A ₁	A ₀	$\overline{Y_0}$	$\overline{Y_1}$	$\overline{Y_2}$	$\overline{Y_3}$	$\overline{Y_4}$	$\overline{Y_5}$	$\overline{Y_6}$	$\overline{Y_7}$
0	x	x	x	x	1	1	1	1	1	1	1	1
x	1	x	x	x	1	1	1	1	1	1	1	1
1	0	0	0	0	0	1	1	1	1	1	1	1
1	0	0	0	1	1	0	1	1	1	1	1	1
1	0	0	1	0	1	1	0	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1	1	1
1	0	1	0	0	1	1	1	1	0	1	1	1
1	0	1	0	1	1	1	1	1	1	0	1	1
1	0	1	1	0	1	1	1	1	1	1	0	1
1	0	1	1	1	1	1	1	1	1	1	1	0

(b) Function Table for 74LS138

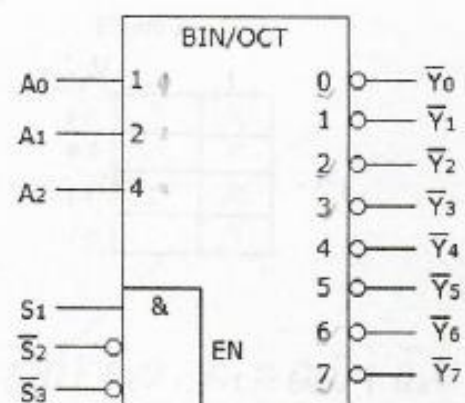

(c) Logic symbol for 74LS138


Figure 1

Truth Table.


A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

AB \ C	0	1
00	1	0
01	1	1
11	1	1
10	0	0
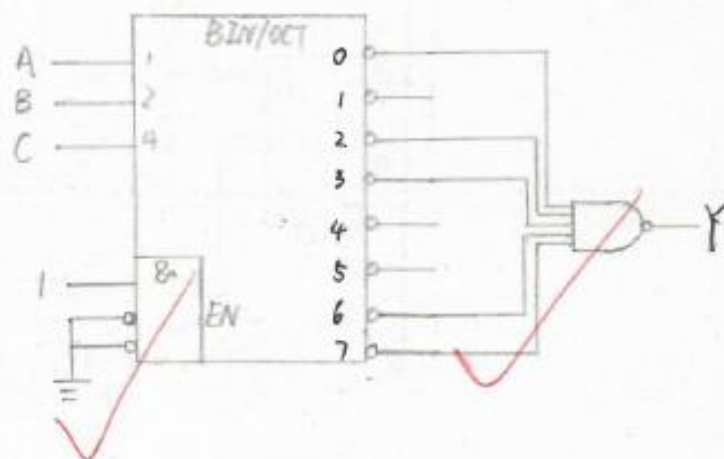
$$\therefore Y = \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C + \overline{A} B \overline{C} + A B \overline{C} + A B C$$




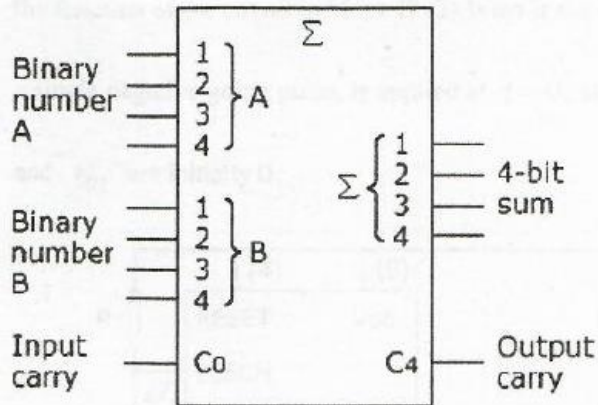4. (10%) Use 4-bit adders to implement a circuit which adds up two 11-bit numbers. Label all critical inputs and outputs.




A 4-bit adder

Figure 2

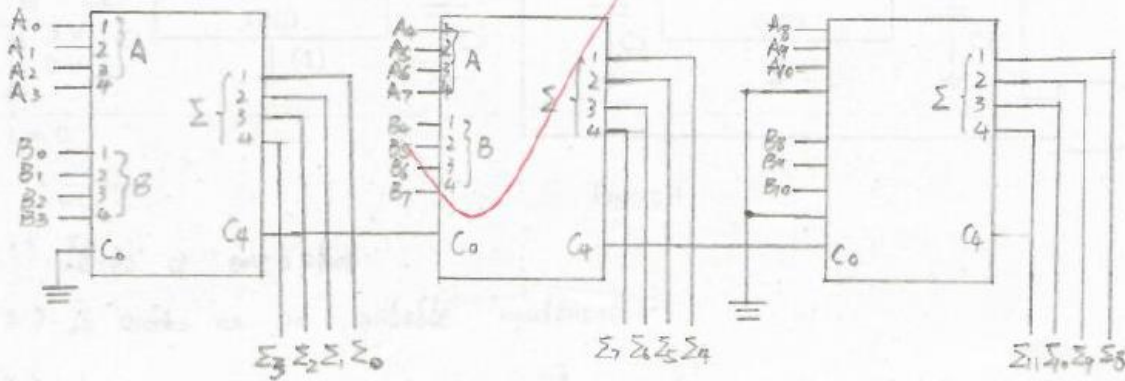

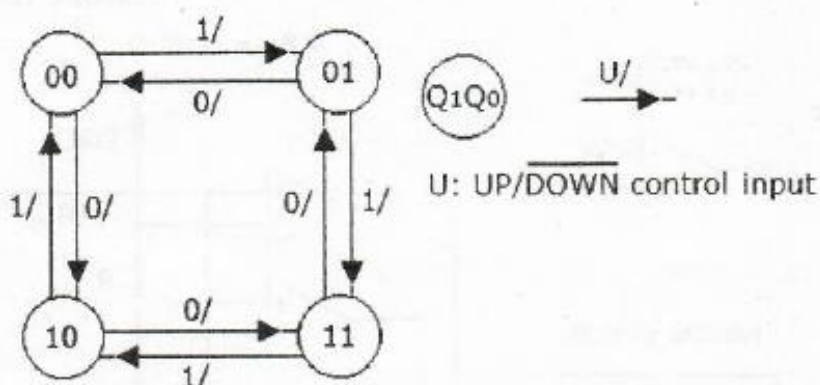5. (15%) Use J-K flip-flops and the minimum number of gates to implement a synchronous 2-bit up/down counter with a Gray code sequence. The counter should count up when an $\overline{\text{UP/DOWN}}$ control input is 1 and count down when the control input is 0.



State diagram for a 2-bit Gray code counter

State table.

$Q_1^n Q_0^n$	$Q_1^{n+1} Q_0^{n+1}$	
	$U=0$	$U=1$
00	10	01
01	00	11
11	01	10
10	11	00


J-K:

$Q^n \rightarrow Q^{n+1}$	J	K
0 0	0	X
0 1	1	X
1 0	X	1
1 1	X	0

Figure 3

$Q_1 Q_0$	U=0	U=1
00	X	X
01	X	X
11	X	X
10	X	X
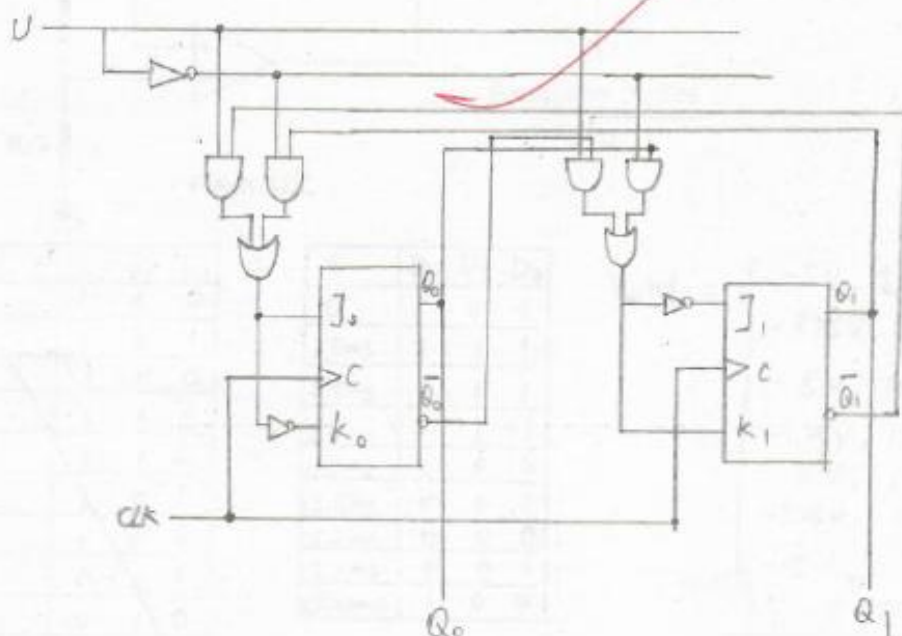
$$J_0 = Q_1 \bar{U} + \bar{Q}_1 U, K_0 = \bar{Q}_1 \bar{U} + Q_1 U, J_1 = \bar{Q}_0 \bar{U} + Q_0 U, K_1 = Q_0 \bar{U} + \bar{Q}_0 U$$



6. (15%) In Figure 4, $R_1 = 150 \text{ k}\Omega$, $R_2 = R_3 = 24 \text{ k}\Omega$, $C_1 = 0.033 \text{ }\mu\text{F}$, $C_2 = C_3 = C_4 = 0.01 \text{ }\mu\text{F}$. (1) What is the function of the circuit in block I? (2) What is the function of the circuit in block II? (3) Suppose that the input v_{IN} , a single negative-going pulse, is applied at $t = 0$, sketch the waveforms v_{O1} , v_{O2} , and v_O . Suppose that both v_{O1} and v_{O2} are initially 0.


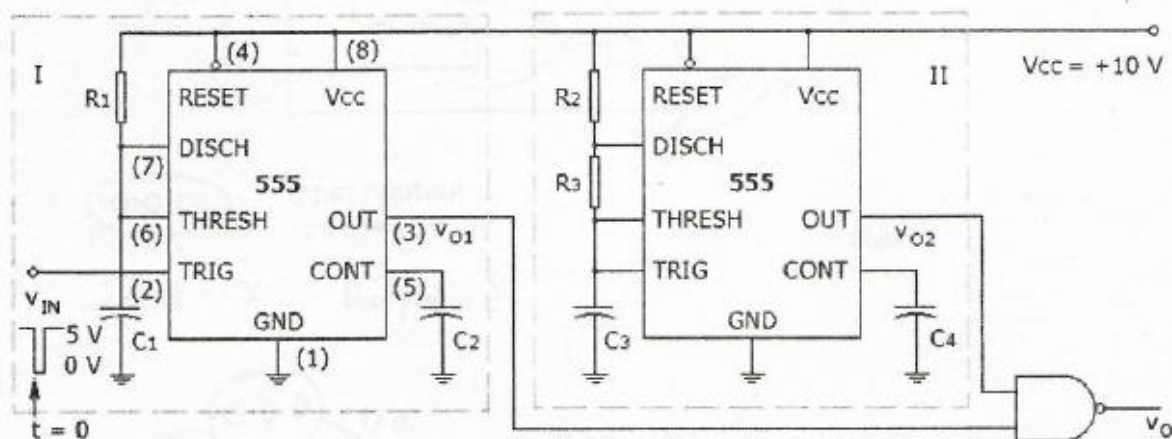


Figure 4

(1) It is a one-shot.

(2) It works as an astable multivibrator.

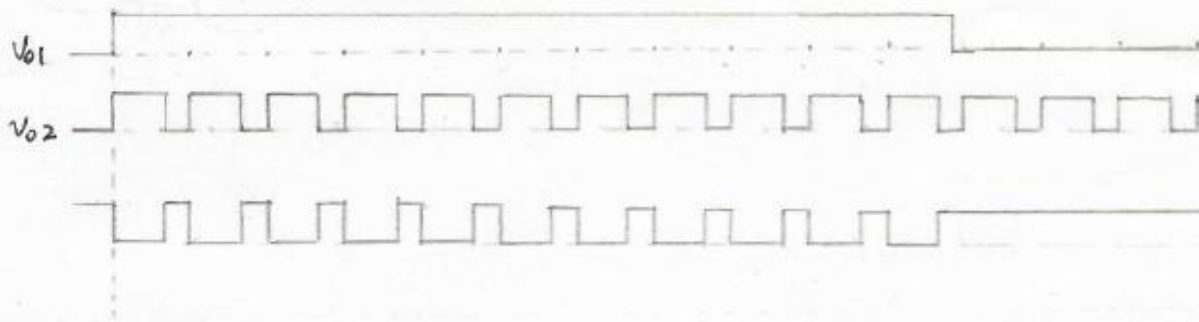(3) $t_{w1} = 1.1 R_1 C_1 = 5.445 \times 10^{-3} \text{ s}$. $t'_{w1} = 0.7 (R_2 + R_3) C_3 = 0.336 \times 10^{-3} \text{ s}$.
 $t'_{w2} = 0.7 R_3 C_3 = 0.168 \times 10^{-3} \text{ s}$. $T = t'_{w1} + t'_{w2} = 0.504 \times 10^{-3} \text{ s}$.



7. (15%) The input to the circuit in Figure 5 is $v_{IN}(t) = 4 + 4\sin(100\pi t)$ V, $0 \leq t \leq 20$ ms. The sampling signal has a frequency of 400 Hz. Determine the binary code sequence $D_2D_1D_0$ and the output $v_{OUT}(t)$ for $0 \leq t \leq 20$ ms.


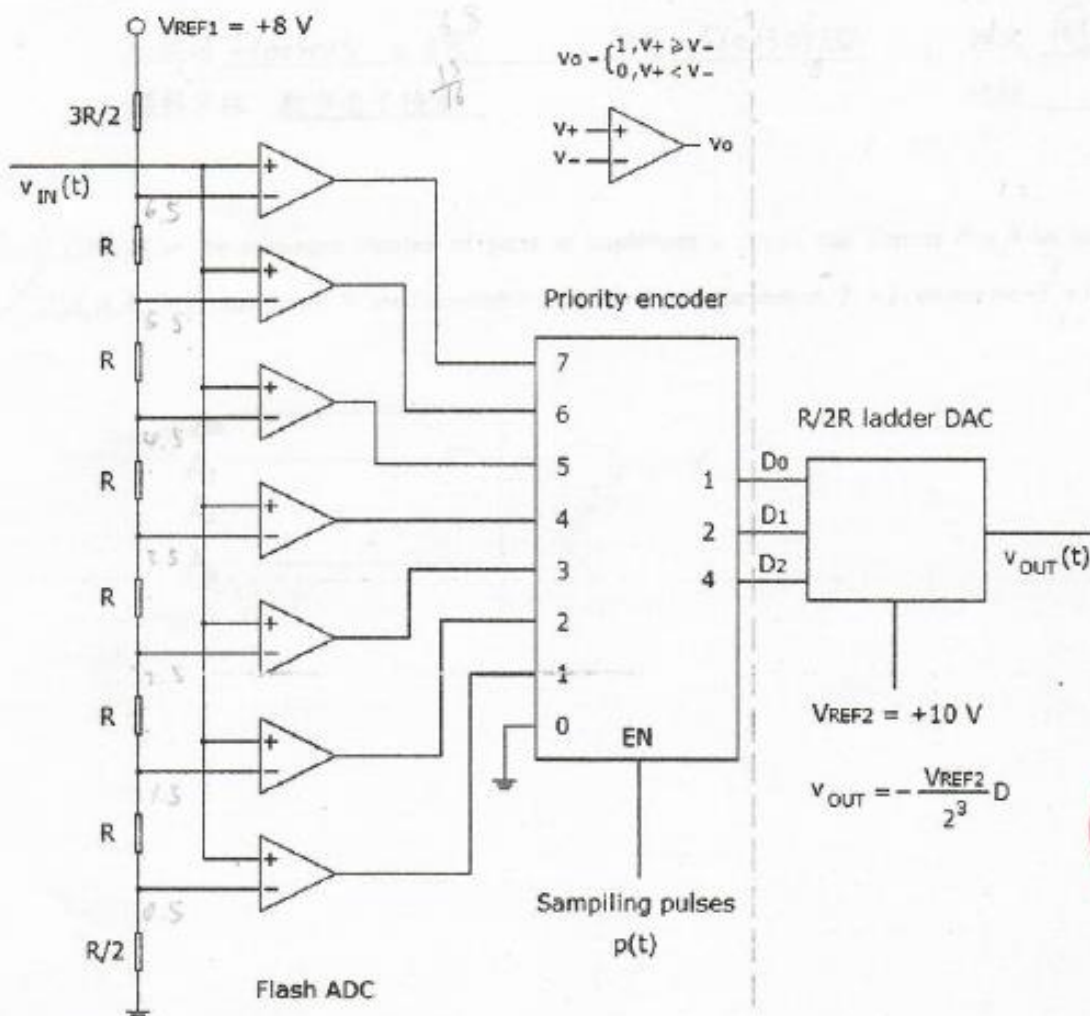


Figure 5

t	D_2	D_1	D_0
0	1	0	0
	1	0	1
	1	1	0
	1	1	1
	1	1	0
	1	0	1
	1	0	0
	0	1	1
	0	1	0
	0	0	1
	0	0	0
	0	0	1
	0	1	0
	0	1	1
	1	0	0

t	D_2	D_1	D_0
0	1	0	0
2.5ms	1	1	1
5.0ms	1	1	1
7.5ms	1	1	1
10.0ms	1	0	0
12.5ms	0	0	1
15.0ms	0	0	0
17.5ms	0	0	1
20.0ms	1	0	0
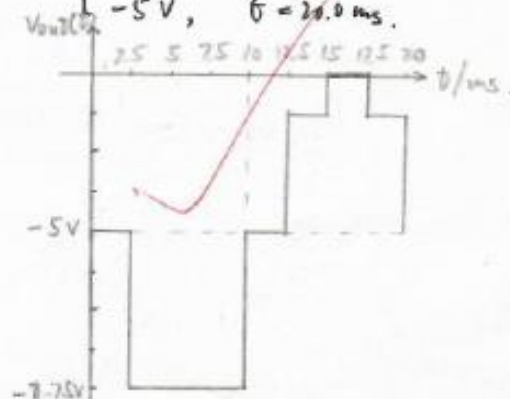
$$V_{out}(t) = \begin{cases} -5V, & 0 \leq t < 2.5\text{ms} \\ -8.75V, & 2.5\text{ms} \leq t < 10.0\text{ms} \\ -5V, & 10.0\text{ms} \leq t < 12.5\text{ms} \\ -1.25V, & 12.5\text{ms} \leq t < 15\text{ms} \\ 0V, & 15\text{ms} \leq t < 17.5\text{ms} \\ -1.25V, & 17.5\text{ms} \leq t < 20.0\text{ms} \\ -5V, & t = 20.0\text{ms} \end{cases}$$



8. (1)


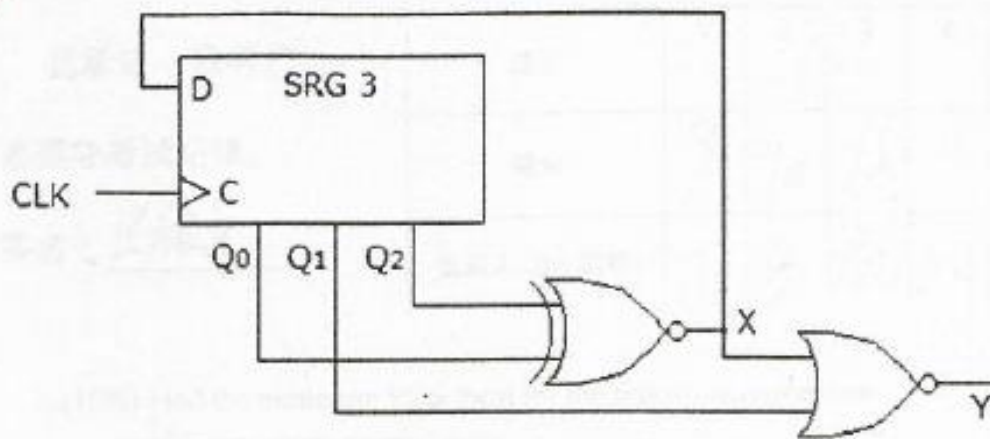


Figure 6

Sol:

Q ₂ Q ₁ Q ₀			Input / Output				
Present state			X	Y	next state		
Q ₂ (n)	Q ₁ (n)	Q ₀ (n)			Q ₂ (n+1)	Q ₁ (n+1)	Q ₀ (n+1)
0	0	0	1	0	0	0	1
0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	1
1	0	1	1	0	0	1	1
0	1	1	0	0	1	1	0
1	1	0	0	0	1	0	0
1	0	0	0	1	0	0	0
1	1	1	1	0	1	1	1

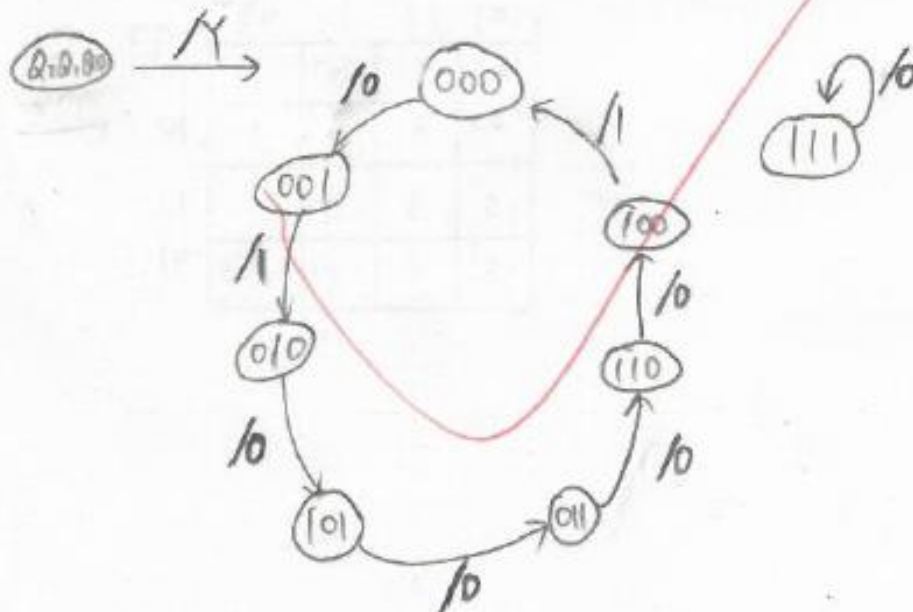

2015-2016 Answer

(I) True/False

FFFTF FTTTF

(II) Choice

BDEAB AABBA

(III) Problem

—.

(III) Problem (60')

一) Using Algebra method to simplify the function. (10')

$$\begin{aligned} F &= xz + \bar{y}z + y\bar{q} + z\bar{q}c + z\bar{q}\bar{c} + x(y + \bar{z}) + \bar{x}yz\bar{q} + x\bar{y}qc \\ &= xz + \bar{y}z + y\bar{q} + z\bar{q}(c + \bar{c}) + x\bar{y} + x\bar{z} + \bar{x}yz\bar{q} + x\bar{y}qc \\ &= x(z + \bar{z}) + \bar{y}z + y\bar{q} + z\bar{q}(1 + \bar{x}y) + x\bar{y} + x\bar{y}qc \\ &= x + \bar{y}z + y\bar{q} + z\bar{q} + x\bar{y} + x\bar{y}qc \\ &= (x + x\bar{y} + x\bar{y}qc) + \bar{y}z + y\bar{q} + z\bar{q} \\ &= x + \bar{y}z + y\bar{q} + z\bar{q} \\ &= x + \bar{y}zq + \bar{y}z\bar{q} + yz\bar{q} + y\bar{z}\bar{q} + yzq + y\bar{z}\bar{q} \\ &= x + \bar{y}zq + \bar{y}z\bar{q} + yz\bar{q} + y\bar{z}\bar{q} \\ &= x + \bar{y}z + y\bar{q} \end{aligned}$$

二) Please use D flip-flop to design a synchronization timing circuit, counter (6 进制计数器);

二.

二) Please use D flip-flop to design a synchronization timing circuit, when $x=0$, the circuit is a sextuple denotation counter (6 进制计数器); when $x=1$, the circuit is a Seven binary counter (7 进制计数器), and when the count value is 101 ($x=0$), or 110 ($x=1$), the output carry is $Z=1$.

Solution: Next State Table.

Q_2^n	Q_1^n	Q_0^n	Q_2^{n+1}	Q_1^{n+1}	Q_0^{n+1}	X	Z	D_2	D_1	D_0
0	0	0	0	0	1	0	0	0	0	1
0	0	1	0	1	0	0	0	0	1	0
0	1	0	0	1	1	0	0	0	1	1
0	1	1	1	0	0	0	0	1	0	0
1	0	0	1	0	1	0	0	1	0	1
1	0	1	0	0	0	0	1	0	0	0
0	0	0	0	0	1	1	0	0	0	1
0	0	1	0	1	0	1	0	0	1	0
0	1	0	0	1	1	1	0	0	1	1
0	1	1	1	0	0	1	0	1	0	0
1	0	0	1	0	1	1	0	1	0	1
1	0	1	0	0	0	1	0	1	0	0
1	1	0	0	1	0	1	0	1	1	0
1	1	1	0	0	0	1	1	0	0	0

数字电子技术 2014-2015 第 1 学期 期末试卷 (A)

共 1 页 6

2. K-map.

Z/Q_0X	Q_2Q_1	00	01	11	10
00	00				
01	01				
11	11	X	1	X	X
10	10				1


D_0/Q_0X	Q_2Q_1	00	01	11	10
00	00	1	1	0	0
01	01	1	1	0	0
11	11	X	0	X	X
10	10	1	1	0	0

D_1/Q_0X	Q_2Q_1	00	01	11	10
00	00	0	0	1	1
01	01	1	1	0	0
11	11	X	0	X	X
10	10	0	0	1	0

D_2/Q_0X	Q_2Q_1	00	01	11	10
00	00	0	0	0	0
01	01	0	0	1	1
11	11	X	0	X	X
10	10	1	1	1	0

$$Z = Q_2Q_1 + Q_2Q_0\bar{X} \quad D_0 = \bar{Q}_2\bar{Q}_0 + \bar{Q}_1\bar{Q}_0 \quad D_1 = \bar{Q}_2\bar{Q}_1Q_0 + \bar{Q}_2Q_1\bar{Q}_0 + Q_2Q_0X$$
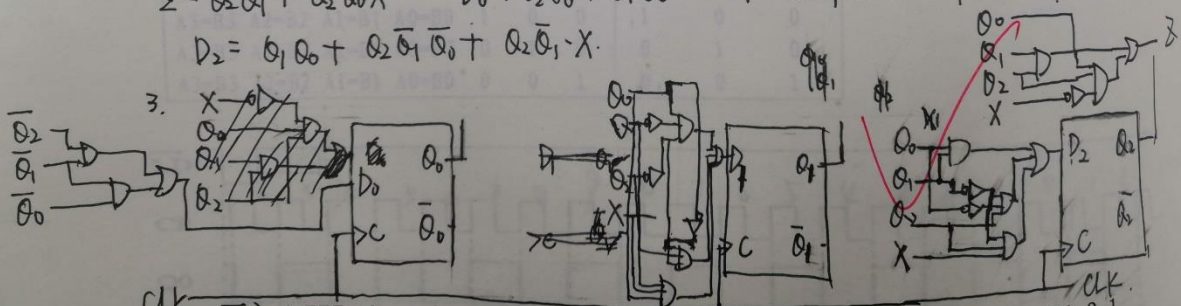
$$D_2 = Q_1Q_0 + Q_2\bar{Q}_1\bar{Q}_0 + Q_2\bar{Q}_1X$$



三) A 555 timer is connected for a stable operation as shown in Fig3-1,

$$t_H = 0.7(R_1 + R_2 + R_3)C$$

$$t_L = 0.7(R_2 + R_3)C$$

$$\therefore P = 3 \sim 3.75$$

$$\therefore \frac{R_1 + R_2 + R_3}{R_1 + R_2 + R_3 + R_2 + R_3} = \frac{3}{5}$$

$$\therefore R_2 = 10 k\Omega$$

$$\therefore t_H = t_L = 0.21 + 0.14 = 0.35 ms$$

$$t_H' = t_H + t_L' = 0.21 + 0.7 \times R_2 C = 0.38 ms$$

$$\therefore 285.71 Hz < f_v < 357.14 Hz$$

四) Analyse the circuit, determine the output waveform. (15')

The 555 timer is used as an astable multivibrator

$$t_H = 0.7(R_1 + R_2)C$$

$$t_L = 0.7(R_2 + R_3)C$$

$$t_H = 0.7(R_1 + R_2 + R_3)C$$

$$t_L = 0.7(R_2 + R_3)C$$

$$P_{bulb} = \frac{V_O^2}{R_{bulb}} \cdot \frac{t_H}{t_H + t_L} = 0.5 \cdot \frac{t_H}{t_H + t_L}$$

$$\therefore \frac{3}{5} \leq \frac{t_H}{t_H + t_L} \leq \frac{3}{4}$$

$$\frac{t_H}{t_H + t_L} = \frac{R_1 + R_2 + R_3}{R_1 + 2R_2 + R_3 + R_3} = \frac{20k + R_2}{20k + 2R_2 + R_3}$$

Then, $t_H = 0.7(30k) \cdot C$
 $= 2.1 \times 10^{-4} s$
 $t_L = 0.7(10k) \cdot C \sim 0.7 \times 10^{-4} s$
 $= 7 \times 10^{-5} s \sim 1.4 \times 10^{-4} s$


$f(V_O) = \frac{1}{t_H + t_L}$
 $= \frac{1}{2.1 \times 10^{-4} + 1.4 \times 10^{-4}}$
 $= 2587.14 \sim 3571.43 Hz$

\therefore for, $R_2 = 10 k\Omega$

四) Analyse the circuit, determine the output waveform. (15')

四.

A3=B3	1	0	x	x	x	x	x	x	0	0	1
A3=B3	A2=B2	0	1	x	x	x	x	x	1	0	0
A3=B3	A2=B2	1	0	x	x	x	x	x	0	0	1
A3=B3	A2=B2	A1=B1	0	1	x	x	x	x	1	0	0
A3=B3	A2=B2	A1=B1	1	0	x	x	x	x	0	0	1
A3=B3	A2=B2	A1=B1	A0=B0	1	0	0			1	0	0
A3=B3	A2=B2	A1=B1	A0=B0	0	1	0			0	1	0
A3=B3	A2=B2	A1=B1	A0=B0	0	0	1			0	0	1

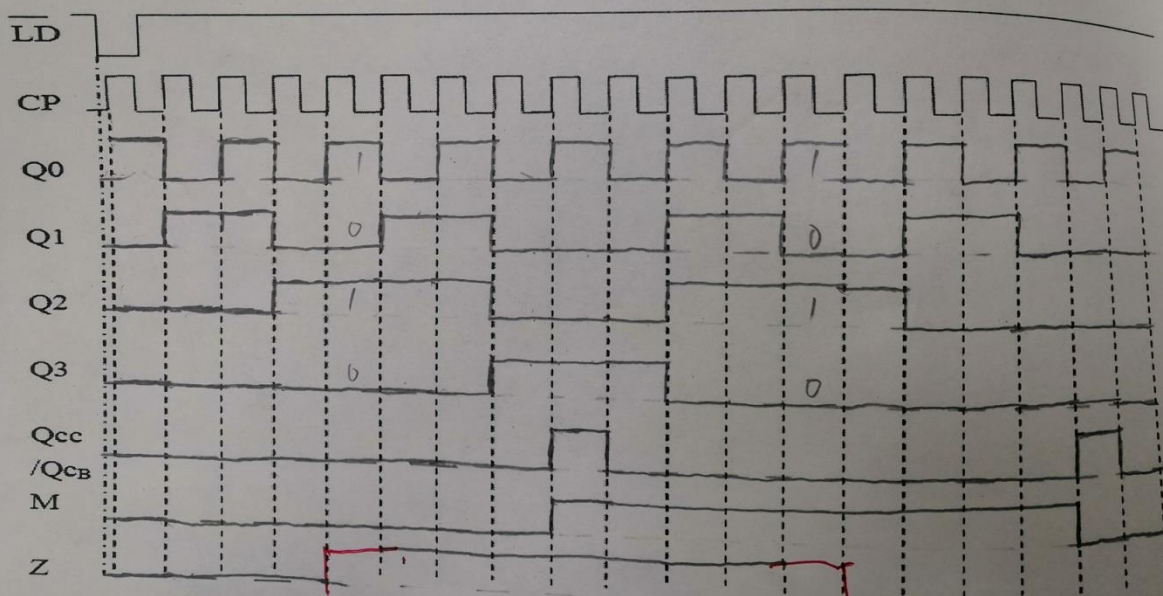

Solution

(2)

五) In Fig3-3 , AD7254 is a 8-bit D/A

五.


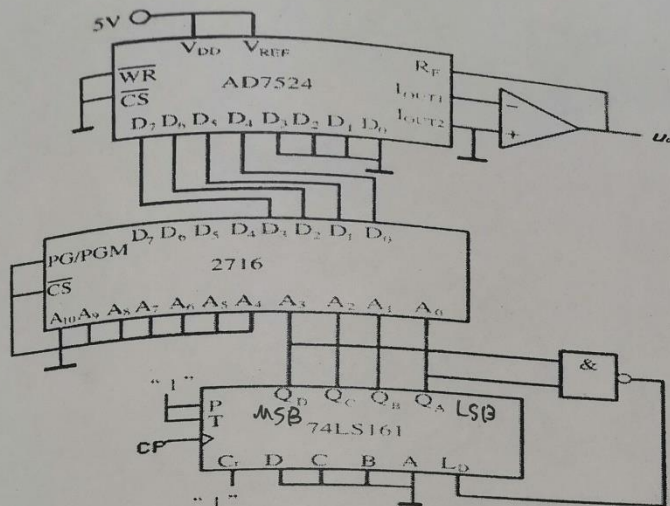


Fig 3-3

地址				数据			
A ₃	A ₂	A ₁	A ₀	D ₇	D ₆	D ₅	D ₄
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	0
0	0	1	1	0	1	1	0
0	1	0	0	1	0	0	0
0	1	0	1	1	0	0	0
0	1	1	0	0	1	1	0
0	1	1	1	0	1	0	0
1	0	0	0	0	0	1	0
1	0	0	1	0	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	1	0
1	1	0	1	0	1	0	0
1	1	1	0	0	0	1	0
1	1	1	1	0	1	0	0

Fig 3-4

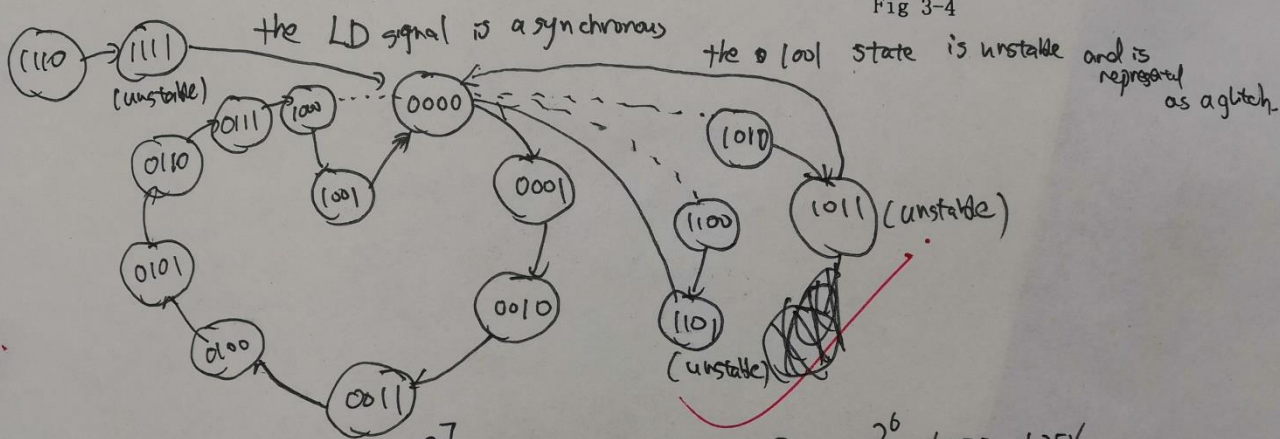

Weight of D₇: $-\frac{2^7}{2^8} \cdot V_{REF} = -2.5V$
D₅: $-\frac{2^5}{2^8} V_{REF} = -0.625V$

D₆: $-\frac{2^6}{2^8} \cdot V_{REF} = -1.25V$
D₄: $-\frac{2^4}{2^8} \cdot V_{REF} = -0.3125V$

